

_____ Go to: <http://www.eia.gov/kids/energy.cfm?page=riddles>

Write 2 riddles:

1. _____

2. _____

CHALLENGE: Come up with a riddle of your own.

Riddle:

Answer:

_____ Go to:

<http://www.sciencekids.co.nz/gamesactivities/electricitycircuits.html>

Follow the directions on the screen to answer the following questions:

1. How did the light bulb grow more brightly?

2. Draw the circuit with the 2 dimly lit light bulbs. Why were they dimmer?

3. How did the coiled wire affect the brightness? Why?

